

# ALTERNATING CURRENT SOLUTIONS

- Q.1.** Given current in a mixture of a d.c. component of 10 A and an alternating current of maximum value 5A.

$$\begin{aligned}\text{R.M.S. value} &= \sqrt{(\text{d.c. current})^2 + (\text{rms value of a.c. current})^2} \\ &= \sqrt{(10)^2 + (5/\sqrt{2})^2} = \frac{15}{\sqrt{2}}.\end{aligned}$$

- Q.2.**  $X_L = 2\pi fL = 2\pi \times 50 \times 0.7 = 220 \Omega$ .

$$z = \sqrt{R^2 + X_L^2} = 220\sqrt{2} \Omega$$

$$\text{Power factor, } \cos \phi = \frac{R}{z} = \frac{220}{220\sqrt{2}} = \frac{1}{\sqrt{2}}.$$

- Q.3.** (a)  $v_{\text{avg}} = \frac{1}{2\pi} \int_0^\pi v_m \sin \alpha d\alpha = \frac{v_m}{2\pi} [-\cos \alpha]_0^\pi = \frac{v_m}{\pi}$

$$v_{\text{eff}} = \frac{1}{2\pi} \left[ \int_0^\pi (v_m \sin \alpha)^2 d\alpha + 0 \right] = \frac{v_m^2}{4}$$

$$\Rightarrow v_{\text{eff}} = \frac{v_m}{2}$$

(b) When switch is closed

$$2 \text{ \& 3 - series} \Rightarrow 2 + 3 = 5 \text{ and } 6 \text{ \& 9 - series} \Rightarrow 6 + 9 = 15$$

$$5 \text{ \& 12 - parallel} \Rightarrow \frac{5 \times 12}{5 + 12} = \frac{60}{17}$$

$$15 \text{ \& } \frac{60}{17} \text{ series} \Rightarrow 15 \times \frac{60}{17} = \frac{315}{17}$$

$$5 \text{ \& 10 parallel} \Rightarrow \frac{10}{3}$$

$$\frac{10}{3} \text{ \& } \frac{315}{17} \Rightarrow \text{are parallel} \Rightarrow \frac{(10/3) \times (315/17)}{\frac{10}{3} + \frac{315}{17}} = 2.825 \text{H}$$

- Q.4.**  $I(t) = \frac{1}{R}(E_1 + E_2)$

$$= \frac{1}{50} (25\sqrt{3} + 25\sqrt{6} \sin \omega t)$$

$$I(t) = \frac{\sqrt{3}}{2} (1 + \sqrt{2} \sin \omega t)$$

Heat produced in one cycle of AC.

$$= \int_0^{2\pi/\omega} I^2(t) R dt = \frac{3}{4} \times 50 \int_0^{2\pi/\omega} (1 + 2 \sin^2 \omega t + 2\sqrt{2} \sin \omega t) dt$$

$$= \frac{75}{2} \left[ \frac{2\pi}{\omega} + \frac{2\pi}{\omega} \right] = \frac{3}{2} \text{ J}$$

No. of cycle in 14 minute is  $N = 14 \times 60 \times 50$


$$\text{Total heat produced} = \frac{3}{2} \times 14 \times 60 \times 50$$

$$\text{Total heat produced} = 3/2 \times 14 \times 60 \times 50 = 63000 \text{ J}$$

**Q.5.** (a)  $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{50}{\pi^2} \times 10^{-2} \times 200 \times 10^{-6}}}$

$\omega_0 = 100 \pi$  (= frequency of impressed voltage)  
hence net current through resistance is zero.

(b)  $v = 5 \sin 100 \pi t$ .

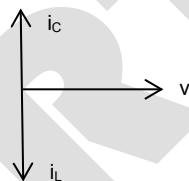

**Q.6.** Comparing,  $E = 100 \sqrt{2} \sin (100 t)$  with  $E = E_{\max} \sin \omega t$ ,  
we get,  $E_{\max} = 100 \sqrt{2} \text{ V}$  and  $\omega = 100 \text{ rad/sec.}$

$$X_C = \frac{1}{\omega C} = \frac{1}{100 \times 10^{-6}} = 10^4 \Omega$$

as ac instrument reads rms value, the reading of ammeter will be,

$$I_{\text{rms}} = \frac{E_{\text{rms}}}{2} = \frac{E_{\max}}{\sqrt{2} X_C} = 10 \text{ mA}$$

**Q.7.** Charged stored in the capacitor oscillates simple harmonically as

$$Q = Q_0 \sin (\omega t \pm \phi)$$

$$Q_0 = 2 \times 10^{-4} \text{ C}$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \times 10^{-3} \times 5 \times 10^{-6}}} = 10^4 \text{ s}^{-1}$$

Let at  $t = 0$ ,  $Q = Q_0$  then,

$$Q(t) = Q_0 \cos \omega t \quad \dots \dots (i)$$

$$i(t) = \frac{dQ}{dt} = -Q_0 \omega \sin \omega t \quad \dots \dots (ii)$$

$$\text{and } \frac{di(t)}{dt} = -Q_0 \omega^2 \cos \omega t \quad \dots \dots (iii)$$

(a)  $Q = 100 \mu\text{C}$  or  $\frac{Q_0}{2}$

from (i) equation  $\cos \omega t = \frac{1}{2}$

from equation (iii)

$$\left( \frac{di}{dt} \right) = Q_0 \omega^2 \cos \omega t$$

$$= 2 \times 10^{-4} (10^4)^2 \times \frac{1}{2}$$

$$\frac{di}{dt} = 10^4 \text{ A/s}$$

- (b)  $Q = 200 \mu\text{C}$  or  $Q_0$  then  $\cos \omega t = 1$  i.e.,  $\omega t = 0, 2\pi, \dots$   
 from equation (ii)  
 $I(t) = -Q_0 \omega \sin \omega t$   
 $I(t) = 0$   
 $[\sin 0 = \sin 2\pi = 0]$

**Q.8.** In one complete cycle

$$I_{av} = 0$$

$$I_{rms} = \sqrt{\frac{\int_0^{\tau/2} \left[ \left( \frac{2I_0}{\tau} \right) t \right]^2 dt}{\int_0^{\tau/2} dt}}$$

$$I_{rms} = \frac{I_0}{\sqrt{3}}$$

**Q.9.** When 'S' is closed

Applying Kirchoff's law

$$0 = iR + (1/C) \int i dt$$

$$i = -(q_0 / RC) e^{-t/RC} = -(40/R) e^{-t/RC}$$

$$\text{but } RC = 0.2 \times 10^6 \times 10 \times 10^{-6} = 2 \text{ sec.}$$

$$\therefore i = \frac{-40}{0.2 \times 10^6} e^{-t/2} = -2 \times 10^{-4} e^{-t/2} \text{ amp.}$$

where -ve sign indicates current is flowing in opposite direction. to our convention.

$$\therefore W_{\text{dissipated}} = \int_0^{\infty} i^2 R dt = \int_0^{\infty} (4 \times 10^{-8}) (2 \times 10^5) e^{-t} dt$$

$$= 8 \times 10^{-3} [e^{-t}]_0^{\infty} = 8 \times 10^{-3} \text{ J.}$$

**Q.10.**  $v = \sqrt{(80)^2 + (60)^2} = 100 \text{ volt,}$

$$\text{p.f.} = \frac{80}{100} = 0.8 \text{ lagging}$$

**Q.11.** The rms value of the current is 1.5 mA

$$\text{The impedance of the capacitor is given by } |Z_C| = \frac{1}{\omega C} = \frac{1}{300 \times 0.5 \times 10^{-6}} \Omega = 6.67 \text{ k}\Omega$$

$$\text{The rms voltage across the capacitor is } 1.5 \times 10^{-3} \times \frac{20}{3} \times 10^3 = 10 \text{ V}$$

The impedance of the circuit is

$$|Z| = \sqrt{(10 \times 10^3)^2 + \left(\frac{20}{3} \times 10^3\right)^2} = 10^3 \times \sqrt{100 + \frac{400}{9}} = 1.2 \times 10^4 \Omega$$

**Q.12.**  $2\pi f\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.5 \times 10^{-3} \times 5 \times 10^{-6})}}$

$$\Rightarrow f = \frac{10^4}{\pi} \text{ Hz}$$

$$\frac{1}{2} cV^2 = \frac{1}{2} Li^2$$

$$5 \times 10^{-6} \times 4 \times 10^4 = 0.5 \times 10^{-7} i^2$$

$$i = 20 \text{ Amp.}$$

**Q.13.**  $X_L = \omega L = \pi \Omega$

$$\text{Impedance} = Z = 3.3 \Omega$$

$$\text{Power factor} = R/Z = 1/3.3$$

**Q.14.**  $C = 0.014 \times 200 \mu \text{ F}$

$$\text{For minimum impedance, } \omega L = 1/\omega C$$

$$L = 0.36 \text{ mH.}$$

**Q.15.** The loop equation

$$\boxed{\boxed{\boxed{\quad}}} L \frac{di}{dt} - iR = 0$$

$$\text{At } t = 0, i = 0,$$

$$60 - 0.008 \frac{di}{dt} = 0$$

$$\frac{di}{dt} = \frac{60}{0.008} = 7500 \text{ A/s}$$

$$\text{Where } \frac{di}{dt} = 500 \text{ A/s, an equation yields,}$$

$$60 - (0.008)(500) - 30i = 0$$

$$30i = 60 - 4 \Rightarrow i = 1.867 \text{ A}$$

$$\text{For the final current } \frac{di}{dt} = 0, \text{ and}$$

$$\boxed{\boxed{\boxed{\quad}}} L(0) - 30 I_F = 0$$

$$I_F = 2 \text{ A}$$

**Q.16.** Applying KVL to the circuit at time 't'

$$2i + \frac{0.2}{10} \frac{di}{dt} = 20$$

$$\text{solving this differential equation :}$$

$$i = 10(1 + 9e^{-100t})$$

**Q.17.** Current in inductance will lag the applied voltage while across the capacitor will lead.

$$I_L = I_{\max} \sin(\omega t - \pi/2) = -0.4 \cos \omega t \text{ for inductor}$$

$$I_C = I_{\max} \sin(\omega t + \pi/2) = +0.3 \cos \omega t \text{ for capacitor}$$

so current drawn from the source.

$$I = I_L + I_C = -0.1 \cos \omega t$$

$$I_{\max} = |I_0| = 0.1 \text{ A.}$$

**Q.18.** Constant value in the cycle therefore

$$V_{\text{avg}} = V_0$$

$$V_{\text{rms}} = V_0$$

**Q.19.**  $v = \sqrt{(80)^2 + (60)^2} = 100 \text{ volt,}$

$$\text{p.f.} = \frac{80}{100} = 0.8 \text{ lagging}$$

**Q.20.** When connected to d.c. source

$$R = \frac{V}{I} = \frac{12}{4} = 3 \Omega \quad \dots(1)$$

When connected to a.c. source

$$Z = \frac{V_{\text{rms}}}{I_{\text{rms}}} = \frac{12}{2.4} = 5 \Omega \quad \dots(2)$$

$$Z = \sqrt{R^2 + (\omega L)^2} \quad \dots(3)$$

From (1), (2) and (3)

$$L = 0.08 \text{ H}$$

with condenser

$$\begin{aligned} Z' &= \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \\ &= \sqrt{3^2 + \left(50 \times 0.08 - \frac{1}{50 \times 2500 \times 10^{-6}}\right)^2} \\ &= 5 \Omega \end{aligned}$$

$$\cos \phi = \frac{R}{Z'} = 0.6$$

$$\begin{aligned} \therefore P &= V_{\text{rms}} \cdot I_{\text{rms}} \cos \phi \\ &= 12 \times 2.4 \times 0.6 = 17.8 \text{ watt} \end{aligned}$$

**Q.21.** (a)  $\tau_L = \frac{L}{R} = \frac{100 \times 10^{-3}}{50} = 2 \times 10^{-3} \text{ sec.}$

$$\therefore \tau = I_0 (1 - e^{t/\tau}) = \frac{V}{R} (1 - e^{t/\tau})$$

$$\frac{dl}{dt} = \frac{V}{\tau R} e^{-t/\tau} = \frac{100}{2 \times 10^{-3} \times 50} \cdot e^{-\frac{0.001}{2 \times 10^{-3}}} \\ = 10^3 (0.606) = 606 \text{ amp/sec.}$$

$$(b) \text{ Heat produced, } H = \int_0^{\tau} I_0^2 (t/\tau)^2 R dt = \frac{1}{3} I_0^2 R \tau$$

$$\therefore I_{\text{rms}} = \sqrt{\frac{(1/3) I_0^2 R \tau}{R \tau}} = \frac{I_0}{\sqrt{3}}$$

**Q.22.** Let effective resistance is  $r$ .

$$\sqrt{3} = \frac{V_c}{rI} \quad \dots (i)$$

$$V_c = \sqrt{3} rI$$

$$\frac{1}{\sqrt{3}} = \frac{V_c}{(rI + 10I)}$$

$$3r = r + 10$$

$$r = 5 \Omega$$

$\therefore$  capacitive nature of box.

**Q.23.** The angular resonance frequency of the circuit is given by:

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \times 10^{-3} \times 10^{-6}}} = 10^4 \text{ rad/s}$$

At a frequency that is 10% lower than the resonance frequency, the reactance  $X_C$ , of the capacitor is:

$$X_C = \frac{1}{\omega C} = \frac{1}{10^4 \times 10^{-6} \times 0.9} \Omega = 111 \Omega$$

And that of the inductance is

$$X_L = \omega L = 10^4 \times 0.9 \times 10^{-2} = 90 \Omega$$

The impedance of the circuit is

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{3^2 + (21)^2} \Omega = 21.2 \Omega$$

$$\text{The current amplitude, } i = \frac{15}{21.2} \text{ A} \approx 0.7 \text{ A}$$

The average power dissipated is:

$$\frac{1}{2} i^2 R = \frac{1}{2} (0.7)^2 \times 3 = 0.735 \text{ W}$$

The average energy dissipated in 1 cycle is

$$0.735 \times \frac{2\pi}{0.9 \times 10^4} \text{ J}$$

$$\text{or } 5.13 \times 10^{-4} \text{ J}$$

**Q.24.**  $\frac{1}{2} L i_0^2 = \frac{1}{2} C v_0^2$

$$i_0 = v_0 \sqrt{\frac{C}{L}}$$

$$v_0 = \frac{q_0}{C} = \frac{5.0 \times 10^{-6}}{4.0 \times 10^{-4}} = 1.25 \times 10^{-2} \text{ volt}$$

$$i_0 = 1.25 \times 10^{-2} \sqrt{\frac{4.0 \times 10^{-4}}{0.09}} = 8.33 \times 10^{-4} \text{ A}$$

$$u_{\max} = \frac{1}{2} Li_0^2 = \frac{1}{2} C v_0^2 = 3.125 \times 10^{-8} \text{ J}$$

$$3.125 \times 10^{-8} = \frac{1}{2} (0.09) \left( \frac{8.33 \times 10^{-4}}{2} \right)^2 + \frac{1}{2} \frac{q^2}{(4.0 \times 10^{-4})}$$

$$q = 4.33 \times 10^{-6} \text{ C.}$$

**Q.25.** At resonance frequency  $f_0 = \frac{1}{2\pi\sqrt{LC}}$

$$i_0 = v_0/R$$

From given condition

$$\frac{1}{\sqrt{2}} \frac{v_0}{R} = \frac{v_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$\omega L - \frac{1}{\omega C} = \pm R.$$

$$2\pi f_1 L - \frac{1}{2\pi f_1 C} = R \quad \dots (i)$$

$$2\pi f_2 L - \frac{1}{2\pi f_2 C} = -R \quad \dots (ii)$$

solving equations (i) and (ii) we get,

$$f_1 - f_2 = \frac{R}{2\pi L}.$$

**Q.26.** 
$$V_{\text{rms}} = \sqrt{\frac{\int_0^T V^2 dt}{\int_0^T dt}} = \sqrt{\frac{\int_0^T \left(\frac{V}{T}\right)^2 t^2 dt}{\int_0^T dt}} = \frac{V}{\sqrt{3}}$$


$$V_{\text{mean}} = \frac{\int_0^T \frac{V}{T} t dt}{T}$$

$$V_{\text{mean}} = \frac{V}{2}$$

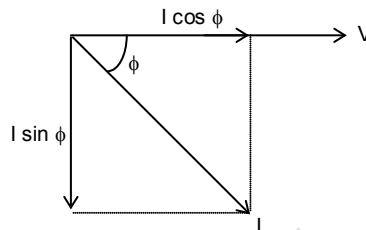**Q.27.** Impedance  $Z = \sqrt{R^2 + \omega^2 L^2}$   
 $= \sqrt{(50)^2 + (2\pi \times 50 \times 0.7)^2}$   
 $= 225.4 \text{ ohms}$   
 $\therefore \text{Current } I = \frac{V}{Z} = \frac{200}{225.4} = 0.887 \text{ amp}$   
and  $\tan \phi = \frac{\omega L}{R} = \frac{2\pi \times 50 \times 0.7}{50} = 4.4$

or  $\phi = 77^\circ 12'$ .

$\therefore$  Power component of current  $IR = I \cos \phi = 0.887 \times \cos 77^\circ 12' = 0.197 \text{ amp.}$   
and wattless components of the current  $I_L$   
 $= I \sin \phi = 0.887 \times \sin 77^\circ 12' = 0.865 \text{ amp.}$



**Q.28.** (i) Applying Kirchhoff's law to meshes (1) and (2)


$$2I_2 + 2I_1 = 12 - 3 = 9$$

$$\text{and } 2I_1 + 2(I_1 - I_2) = 12$$

$$\text{solving } I_1 = 3.5 \text{ A, } I_2 = 1 \text{ A}$$

$$\text{P.D. between AB} = 2I_2 + 3 = 5 \text{ volt}$$
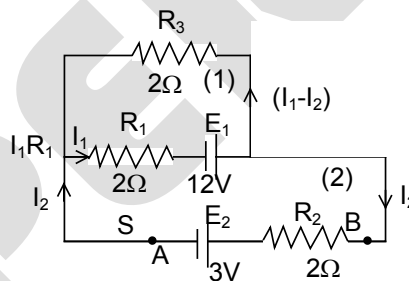
$$\text{Rate of production of heat } \left( \frac{dQ}{dt} \right) = i_1^2 R_1 = 24.5 \text{ (J)}$$



$$(ii) i = \frac{E}{R} [1 - e^{-Rt/L}] = i_0 [1 - e^{-Rt/L}]$$

$$i = i_0/2 \Rightarrow \frac{Rt}{L} = \ln 2$$

$$\Rightarrow t = 0.0014 \text{ sec.}$$

$$\text{Energy stored} = \frac{1}{2} Li^2$$

$$= 0.00045 \text{ (J).}$$